 


Lessons for Test pattern generation

Lesson 1: stuck-at-Faultmodel


Take a look at the following gatelevel netlist:



- Develop a test pattern for the primary inputs A ... D which allows the controllability of a stuck-at-0 fault at node F and the observability at the primary output X.
- Proof your test pattern using a SPICE simulation.

Lesson 2: stuck-short-Faultmodel

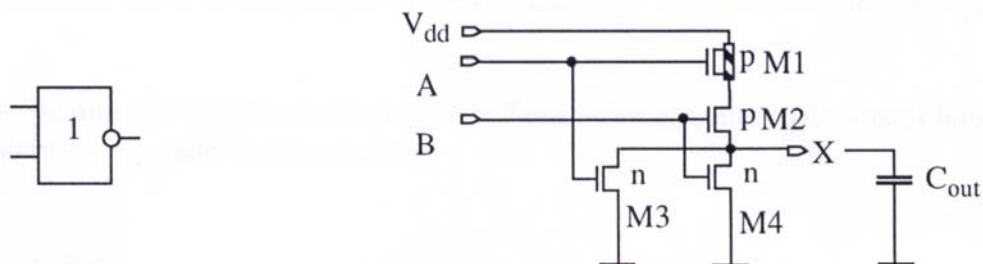
There is a stuck-short fault at D-S at transistor M1 inside a NOR gate.



- Develop a switch-level test to detect this fault
- Check your test pattern in a SPICE simulation. Use a PWL source (piecewise linear voltage) for the stimulation of the inputs. What can you observe at the output (level and current)?

Lesson 3: Complete set of test pattern

Take a look at the following layout:

 

- a) What is the function of this layout? Sketch it as transistor schematic.
- b) Develop a complete set of test pattern for this circuit which allows the detection of all stuck-at-0/1 and of stuck-off/stuck-on faults.
- c) Check your test pattern in a SPICE simulation with the following fault models:
 - a. Stuck-on D-S p1
 - b. Stuck-on D-S n1
 - c. Stuck-off D-S p2
 - d. Stuck-off D-S n2